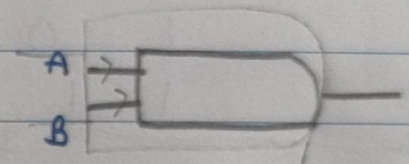


Experiment - 1 Verification of truth's table of Basic gate & Universal gates


AND gate

A	B	$Y = A * B$
0	0	0
0	1	0
1	0	0
1	1	1




OR gate

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

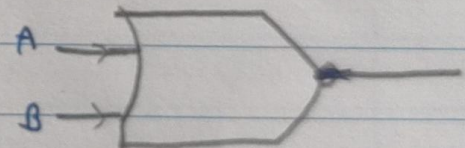

NOR gate

A	B	$Y = A + B$
0	0	1
0	1	0
1	0	0
1	1	0

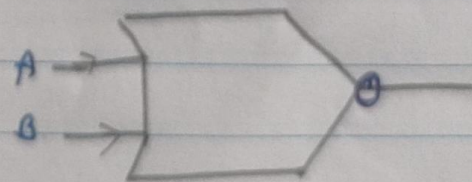


NAND gate

A	B
0	0
0	1
1	0
1	1

$$Y = A * B$$

1
1
1
0

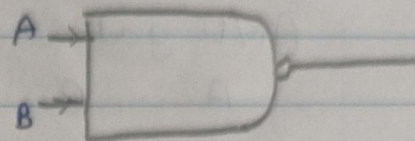


NOT gate

A
0
1

$$Y = \bar{A}$$

1
0

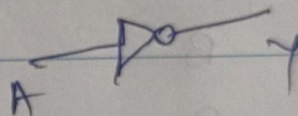

Practical related questions

1) What is logic gate?

→ A logic gate is a fundamental building block of digital circuits. It processes binary inputs based on logical operation.

2) What is the number of not gates in IC 7404?

→ The IC 7404 contains six NOT gates.

3) State the function of pin 7 & 14 of logic gate IC.

→ In a logic gate IC such as 7404, pin 7 is GND (grounded) & pin 14 is VCC (common reference voltage connector).

Ans